

09.21.23 Eðlisfræði 2a

How to deal with BJT circuits?

Note: V_γ is the voltage drop over a forward biased diode. V_{sat} is the saturation voltage.

1. Apply Kirchoff's 2. law ("loop rule") to a closed loop containing the BE junction.
2. Do the same for a loop containing the CE junction.
3. Assume we are in cutoff and set $I_B = 0$ and find V_{BE} based on item 1.
 - (a) If $V_{\text{BE}} < V_\gamma$ then the transistor is in the cutoff region. $I_B = 0$ and V_{BE} remains unchanged. Set $I_C = I_E = 0$ and calculate V_{CE} based on item 2. *Done.*
 - (b) If $V_{\text{BE}} > V_\gamma$ then the transistor is not in cutoff. Set $V_{\text{BE}} = V_\gamma$.
4. Assume the transistor is in the linear region. Set $I_E \simeq I_C \simeq \beta I_B$. Calculate V_{CE} based on item 2.
 - (a) If $V_{\text{CE}} > V_{\text{sat}}$ then the transistor is in the linear region—problem solved.
 - (b) If $V_{\text{CE}} < V_{\text{sat}}$ then the transistor is in saturation. Set $V_{\text{CE}} = V_{\text{sat}}$ and calculate I_C from item 2. Then you should have $I_C < \beta I_B$. Problem solved.

